

24-Oct-2023


Term 4 / Week 3

AC Circuit Analysis

- Let us first consider DC networks to understand the circuit equations for analysis, which are applicable to AC circuits also.

Ex-1

- Consider a simple DC network

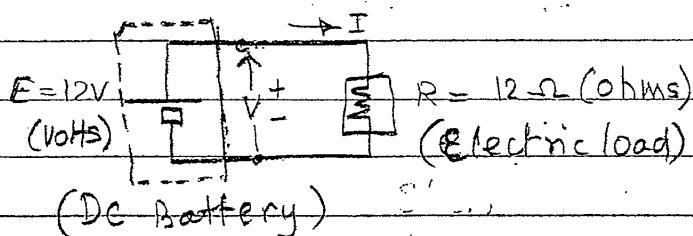

- 2 -

- Using Ohm's law

$$V = IR \quad \text{or} \quad I = \frac{V}{R}$$

$$\text{we have } V = E = 12V \quad \text{&} \quad R = 12\Omega$$


$$\therefore I = \frac{V}{R} = \frac{12V}{12\Omega} = 1A \quad (\text{Ampere})$$

- Ohm's law

- Georg Ohm (German: 1789-1854) experimented with current flow in various lengths of wire!
- school teacher (with Pup!) taught maths & experimented in physics lab. wrote book on geometry to earn a decent income.

- 3 -

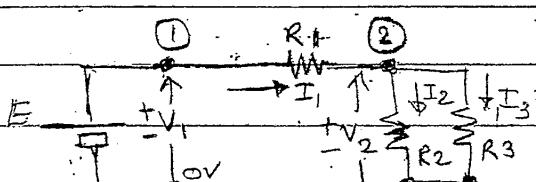- Ex-2 Let us now consider a more general network



| Source | Cable | Loads |

$$\text{Given: } E = 250V, R_1 = 10\Omega \\ R_2 = 100\Omega, R_3 = 4000\Omega$$

Find: Load voltage (V_2) & Total current (I_1)

- In general the above types of problems are solved by using Ohm's at each node with unknown voltage.

- 4 -

- In addition, Kirchoff's law is used at each node
- At each node:

Sum of currents flowing IN = Sum of currents flowing OUT

In general, we can write

$$\sum I_{\text{IN}} = \sum I_{\text{out}}$$

∴ At node (2); we have

$$I_1 = I_2 + I_3$$

Now apply Ohm's law

$$\frac{(V_1 - V_2)}{R_1} = \frac{(V_2 - 0)}{R_2} + \frac{(V_2 - 0)}{R_3}$$

Note: current directions must be assigned, but can be arbitrary!

$$\frac{(250 - V_2)}{10} = \frac{V_2}{100} + \frac{V_2}{400}$$

$$250 - V_2 = 0.1V_2 + 0.025V_2$$

$$250 = V_2 + 0.1V_2 + 0.025V_2$$

$$\therefore V_2 = \frac{250}{1+1.125} = 222.22$$


$$\therefore I_1 = \frac{E - V_2}{R_1} = \frac{250 - 222.22}{10}$$

Ohm's law again!

$$= 2.78 \text{ A}$$

The above is a practical problem — used for sizing the cable so that Load Voltage (V_2) is acceptable!

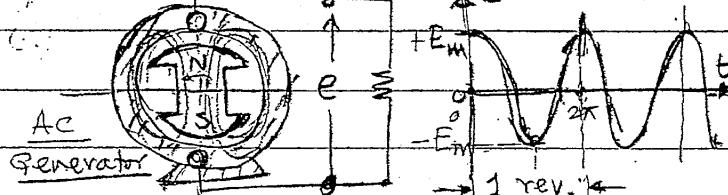- Gustav Kirchhoff (German, 1824-87)
 - Electric circuits, spectroscopy, Black body radiation



A.C. Systems

The generator

- In D.C. systems, voltage and hence the current remain constant with respect to time.

generator

- In A.C. systems, the voltage and hence the current varies sinusoidally w.r.t. time.

- Sinusoidal Variation is obtained by appropriate design of the A.C. generator.

- Hence, the first requirement is to represent the A.C. Voltage & current mathematically.

$$1 \text{ cycle} = 2\pi \text{ radians}$$

$$1 \text{ sec} = 2\pi \times f \text{ radians}$$

$$\therefore t \text{ sec} \Rightarrow 2\pi ft \text{ radians}$$

- We can write that the voltage at any given time 't' as below:

$$1 \text{ revolution} = 1 \text{ cycle}$$

$$e(t) = E_m \cdot \cos(2\pi ft)$$

Volts

$$\therefore 50 \text{ rev/sec} = 50 \text{ cycles/sec}$$

(say "f")

(rev/min) (frequency)

Ex: Given that $E_m = 250 \text{ V}$ & $f = 50$ find the voltage at $t = 0.01 \text{ sec}$.

$$e(t) = E_m \cos(2\pi ft)$$

$$= 250 \cos(2\pi \times 50 \times 0.01)$$

$$= -250 \text{ V} !$$

We need an equation to find the voltage value at any given time, say t sec.