

A.C. Circuit Analysis

- Review

- Ohm's Law  $I = V/R$
- Kirchoff's Current Law (KCL)

$$\sum I_{in} = \sum I_{out}$$

- General Circuit Analysis

- Use KCL at each node with unknown voltage.

- Express branch currents using Ohm's Law.

- The above is applicable for both DC & AC circuit analysis.

- 3 -

1 revolution = 1 cycle

$$\therefore 50 \text{ rev/sec} \Rightarrow 50 \text{ cycles/sec}$$

(3000 rpm)

In general, say, "f" cycles/sec

(where 'f' is called the frequency)

- We need an equation to find the value of the voltage at any given time, say, "t" seconds


- We know that the variation is sinusoidal, and sinusoidal values are calculated using 'sine' or 'cosine' function for a given angle in 'degrees' or 'radians'

- 2 -

A.C. Systems

- In AC systems, the generator voltage (as per design) varies sinusoidally w.r.t. time
- Hence, current also varies sinusoidally w.r.t. time.

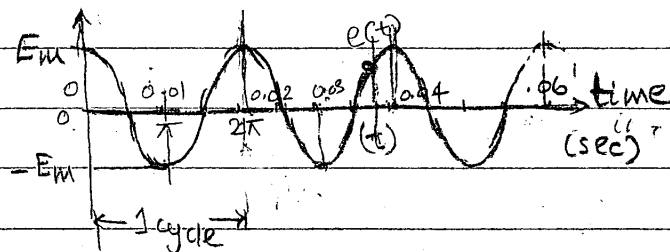- We represent the voltage variation w.r.t. time as below:



1 cycle  $\Rightarrow$  1 revolution of a two-pole generator.

- 4 -

1 cycle =  $2\pi$  radians

Also, 1 second  $\Rightarrow$  'f' cycles

$$\therefore t \text{ sec} \Rightarrow t \times f \times 2\pi \text{ radians}$$

- We can represent the generator voltage at any given time 't'

$$e(t) = E_m \cdot \cos(2\pi ft)$$

Volts

(for the cosine wave shown in the figure.)

Ex: Given that  $E_m = 250V$  and frequency  $f = 50$  cycles/sec, Find voltage at

- (a) 0.01s (b) 0.038s (c) 1.54 sec

we have:

$$e(t) = E_m \cos(2\pi ft) \text{ volts}$$

$$= 250 \cos(2\pi \times 50 \times t)$$

(a)  $t = 0.01 \text{ s}$

$$e(0.01) = 250 \cos(2\pi \times 50 \times 0.01)$$

$$= 250 \cos(\pi)$$

$$= -250 \text{ V}$$

(b)  $t = 0.22 \text{ s}$

$$e(0.22) = 250 \cos(2\pi \times 50 \times 0.22)$$

$$= 250 \cos(11.938)$$


$$= 202.25 \text{ V}$$

(c)  $t = 1.54 \text{ s}$

$$e(1.54) = 250 \cos(2\pi \times 50 \times 1.54)$$


$$= 250 \cos(483.805)$$

$$\approx 250 \text{ V}$$

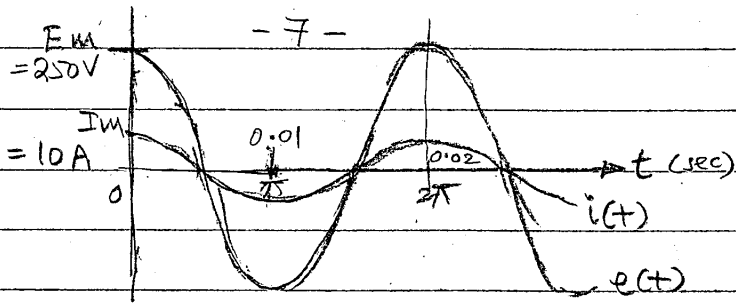

Let us consider another example

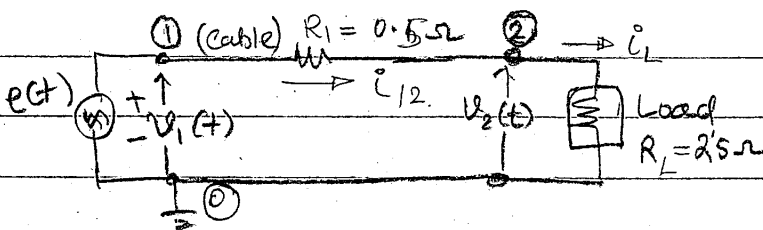
Ex: Find the current in the AC circuit below:



Given  $v_1(t) = e(t) = 240 \cos(2\pi \times 50 \times t)$  Volts

Ex: Calculate the current flowing in the AC circuit below:

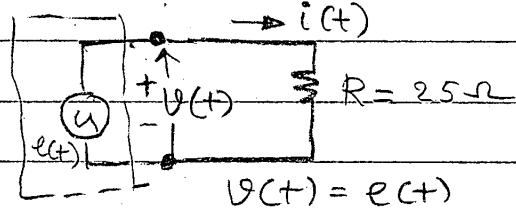Given  $e(t) = 250 \cos(2\pi \times 50 \times t)$  Volts.



(Note: voltage polarity is consistent with current direction. They both change direction every half cycle!)

Using Ohm's law:

$$i(t) = \frac{V(t)}{R} = \frac{250 \cos(2\pi \times 50 \times t)}{25}$$

$$= 10 \cos(2\pi \times 50 \times t)$$

Using KCL:  $i_{12} = i_L$

$$\frac{v_1(t) - v_2(t)}{0.5} = \frac{v_2(t)}{25}$$

Solving we get:

Load Volts:  $v_2(t) = 235.3 \cos(2\pi \times 50 \times t)$  Volts

Load Current:  $i_L(t) = 9.41 \cos(2\pi \times 50 \times t)$  Amps.

However, in A.C. systems, the load voltage  $v_2(t)$  will be much lower due to the voltage drop caused by varying mag. flux! (No such issue in DC!!)

