

7-Nov-2023

Term 4/Week 5

A.c. Circuits - Inductance

• Solution of A.c. circuits becomes more complex (!) due to variation of magnetic field (flux) due voltage and hence current variations.

• The magnetic field (flux) (ϕ) is proportional to current (i)
i.e.

$$\phi \propto i$$

If ' i ' varies sinusoidally then flux (ϕ) also varies sinusoidally.

- 3 -

∴ we have,

$$V_L = \frac{d\phi}{dt} = L \cdot \frac{di}{dt}$$

$$\therefore V_L = L \cdot \frac{di}{dt}$$

• Hence, the solution of A.c. circuits involves solution of differential equations!

• In general, we need to solve multiple (simultaneous) differential equations.

• Let us first consider a single inductance circuit.

• The constant of proportionality can be established and is constant for a given magnetic device (circuit)

• Hence, we can write


$$\phi = L i$$

where L is called the "Inductance" of the given magnetic circuit.

• As per Faraday's Law voltage induced due to varying magnetic field is

$$V_L = \frac{d\phi}{dt}$$

- 4 -

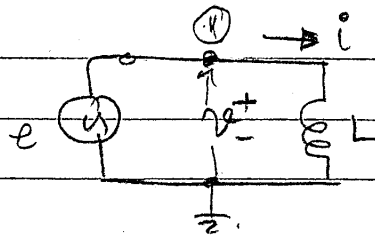

Solve for ' i ' for given

$$e = E_m \cos(2\pi ft)$$

For simplicity let $\omega = 2\pi f$

$$\therefore e = E_m \cos(\omega t)$$

we have


$$e = V = L \cdot \frac{di}{dt}$$

$$\therefore i = \frac{1}{L} \int e dt$$

$$= \frac{1}{L} \int E_m \cos(\omega t) dt$$

• Even though the above integration is straight forward, but in general it is not simple to solve AC networks.

For Ex; for the following circuit

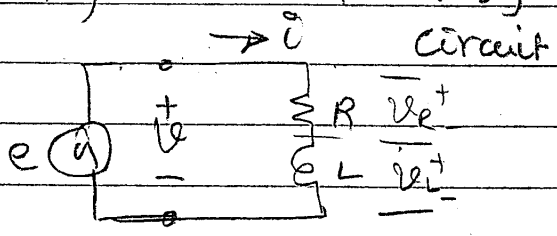

$$e = v = v_R + v_L$$

$$E_m \cos(\omega t) = iR + L \cdot \frac{di}{dt}$$

-solution is not straight forward!!

• There is a much smarter way to solve the above problem - using Complex Numbers!

hence,
$$i = \frac{E_m}{(j\omega)L} e^{j\omega t}$$

$$i = \frac{E_m}{(j\omega L)} e^{j\omega t}$$

$$= I_m e^{j\omega t}$$

$$I_m e^{j\omega t} = \frac{E_m}{j\omega L} e^{j\omega t}$$

$$\therefore I_m = \frac{E_m}{j\omega L}$$

In practice, we are only interested in the "peak" values, since we know all AC waves are sinusoidal.

• Considering our Inductance equation again

$$i = \frac{1}{L} \int E_m \cos(\omega t) dt$$

Let us express $\cos(\omega t)$ as

$$\begin{aligned} \cos(\omega t) &= \text{Real Part of } [e^{j\omega t}] \\ &= \text{Re...} [\cos \omega t + j \sin \omega t]! \end{aligned}$$

Note that we have used $j = \sqrt{-1}$ instead of 'i' since we have used 'i' to represent current.

$$\therefore i = \frac{E_m}{L} \int e^{j\omega t} dt$$

[we can use the "real part" later]

In fact, for Resistance we can write:

$$i = \text{Real Part of } \left[\frac{E_m e^{j\omega t}}{R} \right]$$

$$= I_m \cdot e^{j\omega t}$$

where
$$I_m = \frac{E_m}{R}$$

We now have a general purpose Ohm's law for AC circuits

For Resistance (R) $\Rightarrow I_m = \frac{E_m}{Z}$

where $Z = (R + j0) \cdot e$

& for Inductance (L) $\Rightarrow I_m = \frac{E_m}{Z}$

where $Z = (0 + j\omega L)$

We can now solve for the load Voltage (v_2) for the ex. in week 4.