

A.C. Circuit Solution

• Solution of A.C. Circuits becomes complicated, due to variation of magnetic field (flux) and also variation of electric field (flux) associated A.C. currents & voltages.


• The effect of variation of magnetic field (flux) is modelled (mathematically) by an "Inductance".

-3-

Hence, the current flow

$$i = \frac{dq}{dt} = C \cdot \frac{dV_c}{dt}$$

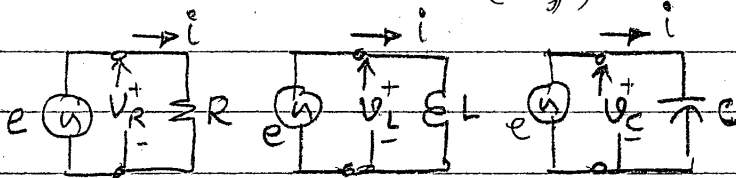• Given $e = E_m \cos(\omega t)$, where $\omega = 2\pi f$



$$i = \frac{E_m \cos(\omega t)}{R} \quad i = \frac{E_m}{L} \int \cos(\omega t) dt \quad i = E_m C \cdot \frac{d(\cos \omega t)}{dt}$$

• The calculations become much simpler, if we replace " $E_m \cos(\omega t)$ " by

$$\cos(\omega t) = \text{Real part of } [E_m e^{j\omega t}]$$

where $j = \sqrt{-1}$

-2-

• We have, voltage drop due to inductance:

$$\mathcal{E}_L = \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$\text{or } i = \frac{1}{L} \int \mathcal{E}_L dt$$

• Similarly, effect of electric field is modelled by a Capacitance.

• We have charge (q) due to electric field due to the voltage (V_c)
 $q = C \cdot V_c$

-4-

• In other words, we replace $E_m \cos(\omega t)$ by the corresponding complex number in Euler's form.

• We can keep "Real part of" at the back of our mind and write

For Resistance

$$i = \left(\frac{E_m}{R}\right) e^{j\omega t}$$

For Inductance

$$i = \frac{E_m}{L} \int e^{j\omega t} = \frac{E_m}{j\omega L} \cdot e^{j\omega t}$$

For Capacitance

$$i = E_m C \frac{d(e^{j\omega t})}{dt} = E_m(j\omega C) e^{j\omega t}$$

• If we are interested only in magnitudes of voltages & currents, we can ignore $e^{j\omega t}$ as it essentially represents sinusoidal variation.
 Hence, it is common to ignore $e^{j\omega t}$ in practice!

∴ we have ; :-

For Resistance

$$I_m = \frac{E_m}{R}$$

For Inductance

$$I_m = \frac{E_m}{j\omega L}$$

For capacitance

$$I_m = \frac{E_m}{(1/j\omega C)}$$

Find load voltage V_L , given that $E = V_s = 240V$ & $f = 50Hz$
 (Note: we are only considering the magnitudes (peak values?) of voltages & currents)

We have:

$$\omega = 2\pi f = 2\pi \times 50 = 314.16$$

Cable impedance

$$\begin{aligned} Z_c &= R + j\omega L \\ &= 0.5 + j314.16 \times 50 \times 10^{-3} \\ &= (0.5 + j15.708) \Omega \end{aligned}$$

Also load impedance:


$$\begin{aligned} Z_L &= (R_L + j0) \\ &= (25 + j0) \end{aligned}$$

Hence, we can now write generalised "Ohm's Law" for A.C.

$$\underline{I}_m = \frac{E_m}{Z}$$

where $Z = (R + j0)$ - Resistance
 $= (0 + j\omega L)$ - Inductance
 $= (0 + \frac{1}{j\omega C})$ - Capacitance
 where Z is called "Impedance"

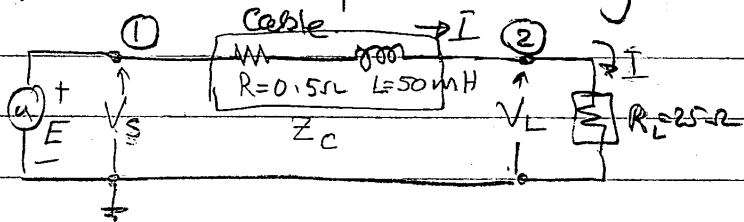Ex: let us now solve the problem in Week 4, by considering inductive drop due to mag. field



Using KCL at node ②

$$\frac{(V_s - V_L)}{Z_c} = \frac{V_L}{Z_L}$$

$$\frac{(240 - V_L)}{(0.5 + j15.708)} = \frac{V_L}{(25 + j0)}$$


Solving, we get

$$V_L = (170.57 - j105.97) V$$

∴ Magnitude of $V_L = |V_L| \approx 200V$

Motor will not start!

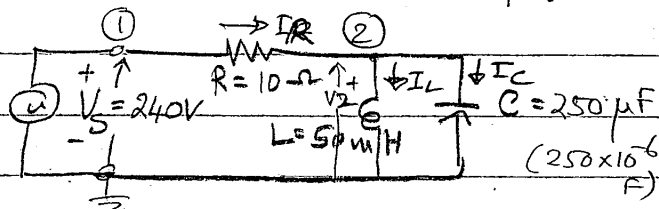Home Work Calculate the voltage at Node 2 (V_2) & currents I_R , I_L & I_C



Ans

$$V_2 = (234.803 - j34.934) I_R = (0.52 - j3.493) I_R = 3.532 A$$

$$I_L = (-2.224 - j14.948) I_C = (2.744 + j18.444) I_C = 18.644 A$$