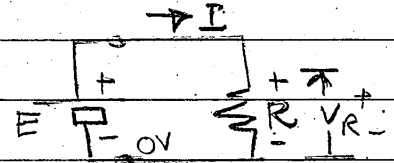


Complex Numbers &
A.C. Circuit Analysis

- Complex numbers help to simplify the solution of Alternating Current (AC) networks.
- Let us first solve Direct Current (DC) networks.
- DC networks have only resistive elements since effects of magnetic and electrostatic fields can be ignored.

• Ohm's law
States that



Voltage drop (V_R) $\frac{1}{2}(R\theta)$
(\equiv Current (I) \times Resistance (R))

or $V_R = I R$ or $I = \frac{V_R}{R}$

(For a given resistor the value of R is a constant)
We have

$E = V_R = I \cdot R$


If $V_S = 12V$ and $R = 6\Omega$

$I = \frac{E}{R} = \frac{12}{6} = 2A$

- If we have two resistances (R_1 & R_2) are connected in series.

Using Ohm's law we have

$V_{R1} = I R_1$
 $V_{R2} = I R_2$

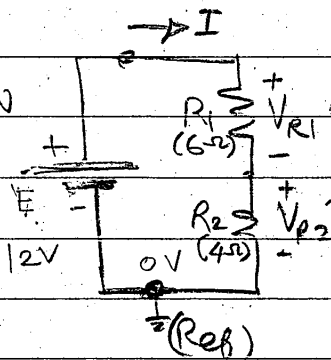

Using Kirchoff's Voltage Law (KVL) - total voltage rise & drop in a closed circuit is zero.

$\therefore +E - V_{R1} - V_{R2} = 0$

$E = V_{R1} + V_{R2} = I R_1 + I R_2$


$\therefore I = \frac{E}{(R_1 + R_2)} = \frac{12}{6 + 4} = 1.2A$

- An AC source or generator voltage varies sinusoidally w.r.t. time.
- This choice makes A.C. systems more efficient!

• Let us say A.C. voltage is

$E(t) = E_m \cos(\theta)$ Volts

where ' θ ' is in radians or degrees.

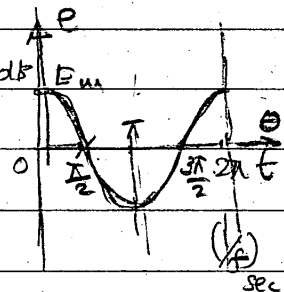

• But, we need to express this as a function of time.

• Let us say there are ' f ' cycles in one second.

$\therefore 2\pi$ radians $\Rightarrow (1/f)$ seconds


$\therefore 1$ second $\Rightarrow 2\pi f$ radians

\therefore At any time ' t ': $E(t) = E_m \cos(2\pi f \cdot t)$ Volts


Ex: Given: $E_m = 100V$ & $f = 50$ cycles/sec
 calculate the voltage at

- (a) 0.0 sec (b) 10 ms (c) 20 ms
- (d) 1.02 s

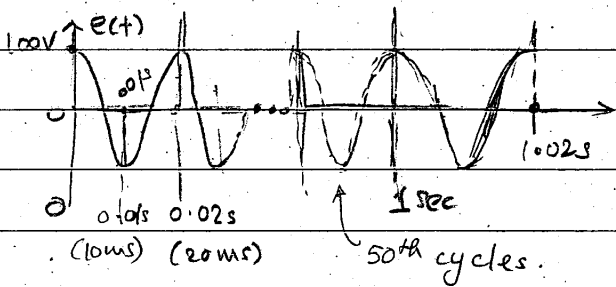(a) $e(0) = 100 \cdot \cos(2\pi \times 50 \times 0) = 100V$
 (b) $e(10ms) = 100 \cdot \cos(2\pi \times 50 \times 10 \times 10^{-3}) = -100V$
 (c) $e(20ms) = 100 \cdot \cos(2\pi \times 50 \times 20 \times 10^{-3}) = 100V$
 (d) $e(1.02s) = 100 \cos(2\pi \times 50 \times 1.02) = +100V$



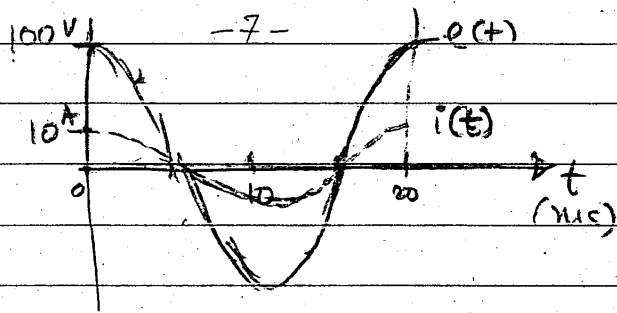Hence the above equation can be used to calculate the voltage at any given time!



Inductance (Effect Magnetic field)

A current flow in a conductor produces a corresponding magnetic flux field. However, in the case of AC, the varying magnetic flux induces a voltage in the same conductor. Such a voltage is given by:

$$V_L = L \cdot \frac{di}{dt} \rightarrow \text{Faraday's Law}$$


'L' (Inductance) is a constant for a given magnetic setup.

Resistance

Solving resistive circuits in AC is straight forward, except that the current also follows the voltage variations.

Ohm's law is

still valid at any given time 't'.

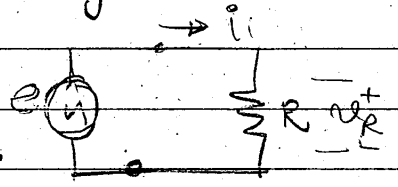

$$V_R = iR$$

$$e = V_R = iR \text{ or } i = \frac{e}{R}$$

Note: $e(t) \equiv e; V_R(t) \equiv V_R$ & $i(t) \equiv i$
 Lower case is used for time varying quantities.


Given $e = E_m \cos(2\pi ft)$ Volts

where $E_m = 100V$ $f = 50$ c/s

for $R = 10\Omega$; $i = \frac{100 \cos(2\pi ft)}{10} = 10 \cos(2\pi ft)$ Amps

Hence we have:

$$e = V_L = L \cdot \frac{di}{dt}$$

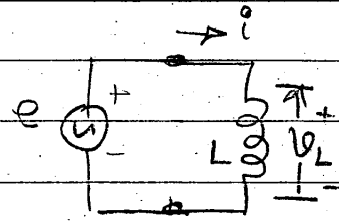

where $e = E_m \cos(2\pi ft)$ volts

$$\therefore i = \frac{1}{L} \int e dt = \frac{1}{L} \int E_m \cos(2\pi ft)$$

A bit difficult but can be solved! $= \frac{E_m}{2\pi fL} \sin(2\pi ft)$

Now let us consider another circuit.


Given $e = E_m \cos(2\pi ft)$, find 'i'
 we have:

$$V_R = iR$$

$$V_L = L \cdot \frac{di}{dt}$$

Also voltage around the loop

$$e - V_R - V_L = 0$$

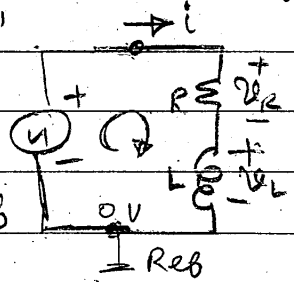

$$\therefore e = V_R + V_L = iR + L \cdot \frac{di}{dt}$$

How do we solve this for 'i'!