

2-Jul-2024

Term 2/Week 10

Complex Numbers & A.C. Circuit Analysis

Review

• DC circuit analysis is done using Ohm's law, namely $\text{Current (I)} = \frac{\text{Voltage (V)}}{\text{Resistance (R)}}$

• A.C. source voltage varies sinusoidally, hence current also varies accordingly.


• Let A.C. source voltage be

$e_s = E_{sm} \cos(2\pi ft)$ volts
where $f = \text{no. of cycles/sec}$

• For Resistance:

Ohm's law

$e_s = \mathcal{V}_R = iR$

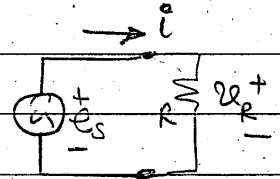


$\therefore i = \frac{e_s}{R} = \frac{E_{sm} \cos(\omega t)}{R}$ Amplitude

(where $\omega = 2\pi f$)


• For inductance (magnetic field)

Faraday's law:

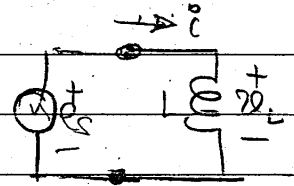$e_s = \mathcal{V}_L = L \cdot \frac{di}{dt}$



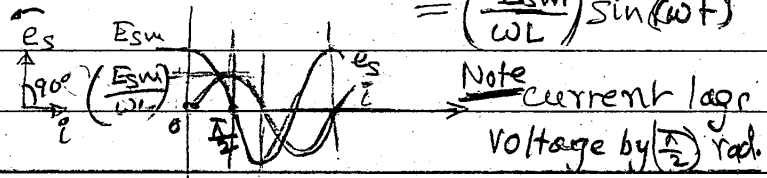
$\therefore i = \frac{1}{L} \int e_s \cdot dt = \frac{1}{L} \int E_{sm} \cos(\omega t) dt$
 $= \left(\frac{E_{sm}}{\omega L} \right) \sin(\omega t)$



Note: current lags voltage by $\left(\frac{\pi}{2}\right)$ rad.

• R-L circuit

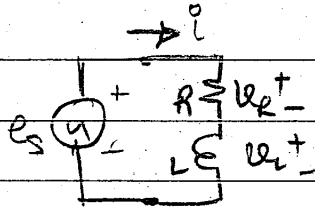$e_s = \mathcal{V}_R + \mathcal{V}_L$
 $= iR + L \cdot \frac{di}{dt}$



This problem becomes difficult to solve! of course, in practice we do have more extensive circuits.

Solution using Complex Numbers

Let us represent the source voltage as a complex number (\bar{E}_s)

$\bar{E}_s = E_{sm} e^{j\omega t}$

(Note: we have used 'j' = $\sqrt{-1}$ instead of 'i' = $\sqrt{-1}$)

Using Euler's equation, we have

$\bar{E}_s = E_{sm} \cos(\omega t) + j E_{sm} \sin(\omega t)$

\therefore source voltage


$e_s = \text{Real Part of } (\bar{E}_s)$

$= E_{sm} \cos(\omega t)$ volts!

Let us now see the advantage (power!) of using complex numbers!

Resistance

Since, the source voltage is a complex

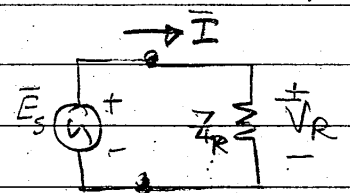

number, let us represent other parameters in the circuit as complex numbers.

Hence, we have:

Current (i) $\Rightarrow \bar{I}$
 Resistance (R) $\Rightarrow \bar{Z}_R = (R + j0)$
 $= R e^{j0}$

Resistor Voltage (V_R) $\Rightarrow \bar{V}_R$

Hence, we have

$$\bar{E}_S = \bar{V}_R = \bar{I} \bar{Z}_R$$

$$\therefore \bar{I} = \frac{\bar{E}_S}{\bar{Z}_R} = \frac{E_{sm} \cdot e^{j\omega t}}{R \cdot e^{j0}}$$

$$= \left(\frac{E_{sm}}{R}\right) e^{j\omega t}$$

$$\therefore i = \text{Real Part of } \left[\frac{E_{sm} \cdot e^{j\omega t}}{R} \right]$$

However, in complex form

we have $\bar{I} = \frac{\bar{E}_S}{\bar{Z}_R}$ ohm's Law for A.C.!

$$\therefore i = \left(\frac{E_{sm}}{\omega L}\right) e^{j(\omega t - \pi/2)}$$

We are interested only in the "Real Part"!

$$\therefore i = \frac{E_{sm}}{\omega L} \cos(\omega t - \pi/2)$$

$$i = \frac{E_{sm}}{\omega L} \sin(\omega t) \text{ Amps}$$


Same result as before for Inductance!

However, it is much simpler to leave the values in complex form by replacing the inductance 'L' as a complex number, namely "j ω L".
 i.e., Inductance (L) $\Rightarrow Z_L = (0 + j\omega L)$

Inductance

Recall that

$$e_s = v_L = L \cdot \frac{di}{dt}$$

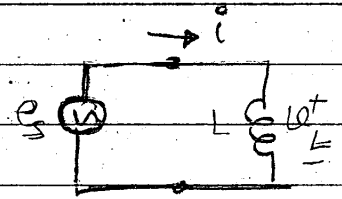

we now have:

$$P_s = \text{Real Part of } (E_{sm} e^{j\omega t})$$

$$\therefore i = \frac{1}{L} \int e_s dt = \frac{1}{L} \int E_{sm} e^{j\omega t} dt$$

Notes let us keep "Real Part of" in the back of our mind!

we have, after integration

$$i = \frac{1}{(L)(j\omega)} E_{sm} \cdot e^{j\omega t}$$

$$= \frac{E_{sm} e^{j\omega t}}{(j\omega L)} = \frac{E_{sm} e^{j\omega t}}{\omega L e^{j(\pi/2)}}$$

using complex values:

$$\bar{E}_S = E_{sm} e^{j\omega t} \text{ volts}$$

$$\bar{Z}_L = (0 + j\omega L)$$

$$= \omega L e^{j\pi/2}$$

\therefore we have

$$\bar{I} = \frac{\bar{E}_S}{\bar{Z}_L} \text{ or } \frac{E_{sm} e^{j\omega t}}{\omega L e^{j\pi/2}}$$

This form is more convenient

Also, we have

$$\bar{V}_L = \bar{E}_S$$

\therefore for inductance, we can write

$$\bar{I} = \frac{\bar{V}_L}{\bar{Z}_L}$$

Ohm's Law for Inductance

\therefore we can solve AC Circuits similar to DC!!

"in A.C.!"