

30-JUL-2024

Term 3 / Week 2

Complex Numbers in A.C. Circuit Analysis

A.C. Source

- An A.C. Source voltage ( $e_s$ ) varies sinusoidally wr.t. time.
- Let us say that the number of sinusoidal cycles/second is 'f'
- We can represent the sinusoidal variations mathematically as below:


$$e_s = e_s(t) = E_{sm} \cdot \cos(2\pi ft)$$

[In practice, ' $e_s$ ' is treated as identical to ' $e_s(t)$ ']

-3-

A.C. source connected to Resistance

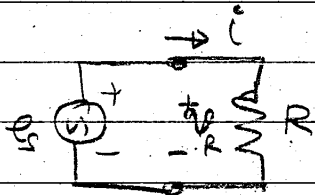- Note that lower case variables represent time varying values.



- Also, " $2\pi f$ " is denoted by " $\omega$ "
- ∴ we have:

$$e_s = E_{sm} \cos(\omega t) \text{ volts}$$


$$V_R = iR \text{ - ohm's law}$$

$$e_s - V_R = 0 \text{ - Kirchoff's Voltage Law (K.V.L.)}$$

$$\therefore e_s = V_R = iR$$

$$\text{or } i = \frac{e_s}{R} = \frac{E_{sm} \cos(\omega t)}{R}$$
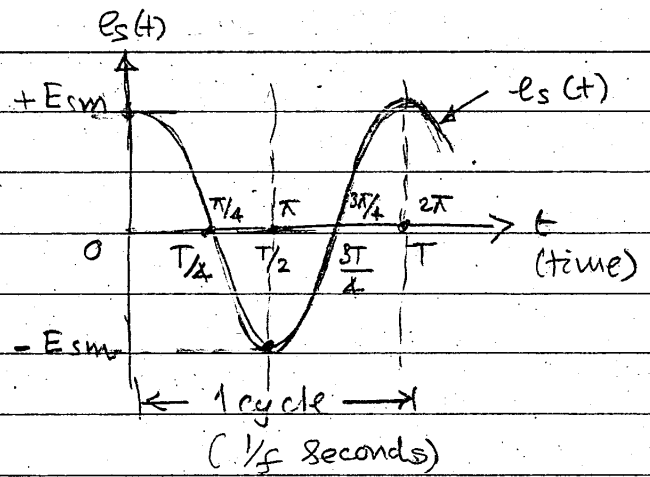
$$\therefore i = \left(\frac{E_{sm}}{R}\right) \cos(\omega t) = I_m \cos(\omega t)$$



- time for one cycle ( $T$ ) =  $1/f$  sec.

For ex: given  $f = 50 \text{ Hz}$  &  $E_{sm} = 100 \text{ V}$

the values of voltage at time  $t = 10 \text{ ms}$  or  $10 \times 10^{-3}$  second

$$\begin{aligned} e_s(10 \text{ ms}) &= E_{sm} \cos(2\pi \times 50 \times 10 \times 10^{-3}) \\ &= 100 \cos(\pi) \\ &= -100 \text{ V} \end{aligned}$$

-4-

where, ' $I_m$ ' is the maximum value of the current

$$\therefore I_m = \left(\frac{E_{sm}}{R}\right)$$


- the current ' $i$ ' follow "cosine" wave in phase with ' $e_s$ '.
- Hence, the solution of AC circuits with Resistor is straight forward.
- We do not need complex numbers!

A.C. source connected to Inductance

Given ' $e_s$ ' & ' $L$ '

Solve for ' $i$ '

We have:

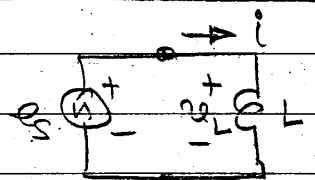

$$e_s = E_{sm} \cos(\omega t)$$

$$V_L = L \cdot \frac{di}{dt} \text{ - Faraday's law}$$

-5-

Also  $e_s = v_L = 0$  — K.V.L.

we have

$$e_s = v_L = L \cdot \frac{di}{dt}$$

$$\therefore i = \frac{1}{L} \int e_s dt = \frac{1}{L} \int E_{sm} \cos(\omega t) dt$$

Integration becomes much easier if we express

$$e_s = \text{Real Part of } [E_{sm} e^{j\omega t}]$$

$$E_{sm} e^{j\omega t} = \underbrace{E_{sm} \cos(\omega t)}_{\text{Real Part}} + j E_{sm} \sin(\omega t)$$

$$\therefore i = \frac{1}{L} \int E_{sm} e^{j\omega t} dt$$

Note: we can use only the "Real Part" after integration!

$$i = \frac{E_{sm}}{j\omega L} e^{j\omega t} \quad \left[ \begin{array}{l} \text{Note:} \\ \int e^{ax} dx = \frac{1}{a} e^{ax} \end{array} \right]$$

-7-

At time  $t=0$ , Eqn (1) becomes

$$i = \frac{E_{sm} e^{j0}}{X_L e^{j90^\circ}}$$

By treating the above equation complex numbers, we have

$$\bar{I} = \frac{\bar{E}_s}{\bar{Z}_L} \Rightarrow \text{Ohm's law (in complex form)}$$

$$\text{Where } \bar{E}_s = E_{sm} e^{j0} \text{ \& } \bar{Z}_L = X_L e^{j90^\circ} \\ = (E_{sm} + j0) = (0 + jX_L)$$

Hence, our problem is now transformed from a Differential Equation to an Algebraic Equation.

(but with complex numbers!)

This makes solution of general AC circuits much simpler.

-6-

$\therefore$  we have

$$i = \frac{E_{sm} e^{j\omega t}}{j\omega L} \quad (\text{let } X_L = \omega L)$$

$$\boxed{i = \frac{E_{sm} e^{j\omega t}}{X_L e^{j90^\circ}}} \quad \text{--- Eqn (1)}$$

$$\text{Hence } i = \text{Real Part} \left[ \frac{E_{sm}}{X_L} e^{j(\omega t - 90^\circ)} \right]$$

$$\text{i.e., } i = \frac{E_{sm}}{X_L} \cos(\omega t - 90^\circ) \text{ at time 't'}$$


The current ( $i$ ) through the inductance is a "cosine" wave with a phase lag of  $90^\circ$  to voltage ( $e_s$ )

Since, both ' $e_s$ ' & ' $i$ ' are "cosine" waves, they can be constructed by knowing only the values at  $t=0$ !

-8-

Ex: Given  $e_s = 100 \cos(\omega t)$  &  $f = 50$  Hz  
and  $L = 10$  mH

Calculate the current flow ( $i$ )

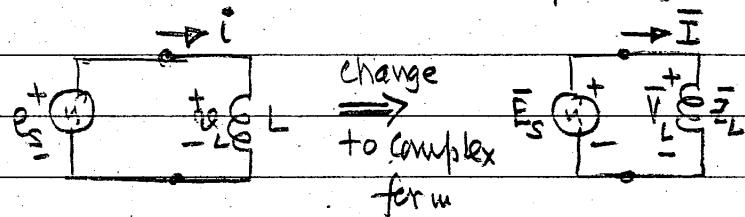

We have:  $\bar{E}_s = E_{sm} e^{j0} = 100 e^{j0}$   
 $\bar{Z}_L$  in Polar form  $\Rightarrow = 100 \angle 0^\circ$  V

$$\bar{Z}_L = X_L e^{j90^\circ} = (\omega L) e^{j90^\circ} \\ = (2\pi f L) e^{j90^\circ} \\ = (2\pi \times 50 \times 10 \times 10^{-3}) e^{j90^\circ} \\ = 3.1416 e^{j90^\circ} = 3.1416 \angle 90^\circ$$

$$\therefore \bar{I} = \frac{100 \angle 0^\circ}{3.1416 \angle 90^\circ} = 31.83 \angle -90^\circ \text{ A}$$

$$\text{At } t=0: i = \text{Real Part} [\bar{I}] = 31.83 \cos(-90^\circ)$$

$$\text{At any 't' } i = 31.83 \cos(\omega t - 90^\circ) \text{ Amps}$$