


13-Jul-2024

Term 3 / Week 4

A.C. Circuit Examples

Inductance (Traditional Method)

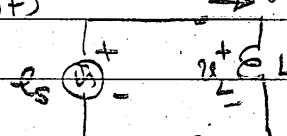Given $e_s = E_{sm} \cos(\omega t)$ & $\omega = 2\pi f$
 and L , find 'i'
 we have,



$e_s = v_L = L \cdot \frac{di}{dt}$ - Faraday's Law


$\therefore i = \frac{1}{L} \int e_s dt = \frac{1}{L} \int E_{sm} \cos(\omega t) dt$

$i = \frac{E_{sm}}{\omega L} \sin(\omega t)$

Ex. 1 Given $E_{sm} = 100V$, $f = 50Hz$
 and $L = 10mH$, calculate 'i'.

we have, $E_{sm} = 100V$, $L = 10mH = 10 \times 10^{-3}H$
 $\omega = 2\pi f = 2\pi \times 50 = 100\pi$

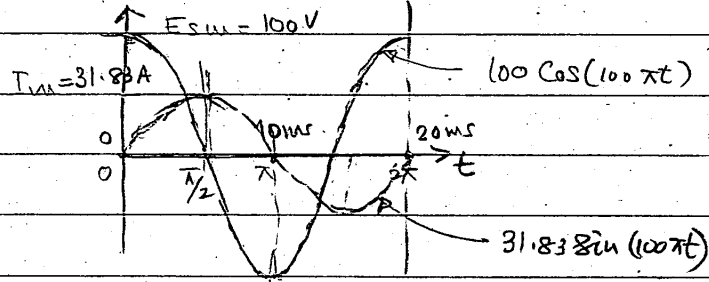$\therefore i = \frac{100}{(100\pi) \times (10 \times 10^{-3})} \sin(\omega t)$
 $= 31.83 \sin(100\pi t)$ Amps.



Note that (peak value of) current lags the (peak value of) voltage by $\pi/2$ radians or 90° .

Inductance (Complex No. Method)

To express 'e' in complex form $\rightarrow i$

let $\bar{E}_s = E_{sm} \cdot e^{j\omega t}$

$= E_{sm} \cos(\omega t) + j E_{sm} \sin(\omega t)$

Real Part

$\therefore e_s = \text{Real Part of } (\bar{E}_s \text{ or } E_{sm} e^{j\omega t})$
 $= E_{sm} \cos(\omega t)$

Using circuit equations

$e_s = v_L = L \cdot \frac{di}{dt}$

$i = \frac{1}{L} \int e_s dt$

$= \text{Real Part of } \left[\frac{1}{L} \int E_{sm} e^{j\omega t} \right]$

$= \text{Real Part of } \left[\frac{1}{j\omega L} \cdot E_{sm} e^{j\omega t} \right]$

Expressing as complex variables:

$\bar{I} = \frac{\bar{E}_s}{\bar{Z}_L} = \frac{E_{sm} \cdot e^{j\omega t}}{(\omega L) e^{j90^\circ}}$

Note:
 let $\bar{Z}_L = \omega L e^{j90^\circ}$

$= \frac{E_{sm}}{\omega L} e^{j(\omega t - 90^\circ)}$


$\therefore i = \text{Real part of } (\bar{I})$
 $= \left(\frac{E_{sm}}{\omega L} \right) \cos(\omega t - 90^\circ)$

$i = \left(\frac{E_{sm}}{\omega L} \right) \sin(\omega t)$

Ex 2

Solve Example 1 using complex variables;

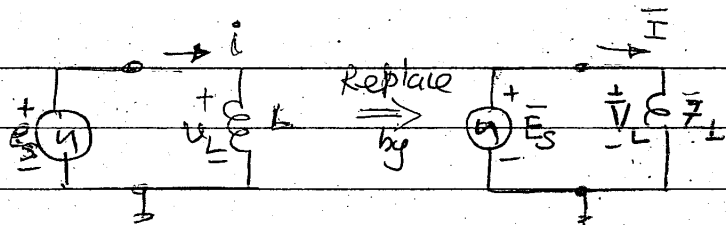Let us replace our circuit with complex variables;



In complex form we have

$$\begin{aligned} \bar{E}_s &= 100 e^{j\omega t} \text{ Volts} \\ \bar{Z}_L &= (\omega L) e^{j90^\circ} \text{ ohms} \\ &= (2\pi f L) e^{j90^\circ} \\ &= (2\pi \times 50 \times 10 \times 10^{-3}) e^{j90^\circ} \\ &= (\pi) e^{j90^\circ} \text{ ohms} \end{aligned}$$

∴ current in complex form

$$\begin{aligned} \bar{I} &= \frac{\bar{E}_s}{\bar{Z}_L} = \frac{100 e^{j\omega t}}{(\pi) e^{j90^\circ}} \\ &= 31.83 e^{j(\omega t - 90^\circ)} \text{ Amps} \end{aligned}$$

∴ the actual current

$$\begin{aligned} i &= \text{Real part of } (\bar{I}) \\ &= \text{Real Part of } [31.83 \cos(\omega t - 90^\circ) \\ &\quad + j 31.83 \sin(\omega t - 90^\circ)] \end{aligned}$$

$$\begin{aligned} \therefore i &= 31.83 \cos(\omega t - 90^\circ) \\ &= \underline{31.83 \sin(\omega t)} \quad !! \end{aligned}$$

• Same result as before, but no integration was necessary!

• Inductance ^{Equation} can now be treated as algebraic equation instead of differential equation

• We can replace time dependent equation

$$e_s = v_L = L \frac{di}{dt}$$

by complex equation


$$\bar{E}_s = \bar{V}_L = \bar{Z}_L \cdot \bar{I}$$

$$\text{or } \bar{I} = \frac{\bar{E}_s}{\bar{Z}_L} = \frac{\bar{V}_L}{\bar{Z}_L}$$

where $\bar{Z}_L = j\omega L$ or $\omega L e^{j90^\circ}$

Ex: 3

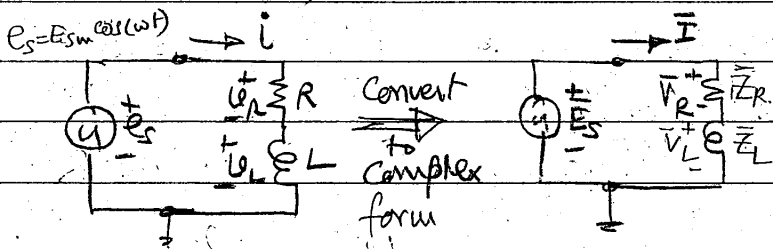Given $E_{sm} = 100V$, $f = 50Hz$, $R = 10\Omega$, $L = 10mH$, calculate current 'i'.



We have: $\omega = 2\pi f = 2\pi \times 50 = 100\pi$

$$\begin{aligned} \bar{E}_s &= E_{sm} e^{j\omega t} = 100 e^{j100\pi t} \text{ V} \\ \bar{Z}_R &= 10\Omega = 10 e^{j0} \Omega \\ \bar{Z}_L &= \omega L e^{j90^\circ} = 3.1416 e^{j90^\circ} \Omega \end{aligned}$$

Using K.V.L. for the circuit

$$\bar{E}_s = \bar{V}_R + \bar{V}_L = \bar{I} \bar{Z}_R + \bar{I} \bar{Z}_L$$

$$\begin{aligned} \therefore \bar{I} &= \frac{\bar{E}_s}{\bar{Z}_R + \bar{Z}_L} = \frac{100 e^{j\omega t}}{10 e^{j0} + 3.1416 e^{j90^\circ}} \\ &= \frac{100 e^{j\omega t}}{(10 + j0) + (0 + j3.1416)} \\ &= \frac{100 e^{j\omega t}}{10.482 e^{j17.44^\circ}} = \underline{9.54 e^{j(\omega t - 17.44^\circ)}} \text{ Amps} \end{aligned}$$

∴ The actual current is

$$\begin{aligned} i &= \text{Real Part of } [\bar{I}] \\ &= \underline{9.54 \cos(\omega t - 17.44^\circ)} \text{ Amps} \end{aligned}$$

∴ current (peak) lags voltage (peak) by 17.44!